 
 


Given:

Find: Excitation table for a) & b). Simplify equations, if possible and comment on the effect of feedback

Solution

a)

Q	X	Y	Q*
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

xy \ Q		Q*	
		0	1
0	0	1	1
	1	1	1
1	0	0	0
	1	0	0

$$Q^* = \overline{X}$$

The feedback has no effect on Q\*

b)

Q	X	Y	Q*
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

xy \ Q		Q*	
		0	1
0	0		1
	1		
1	0	1	1
	1		1

$$Q^* = Q\overline{Y} + XY$$

The feedback forces Q\* to High unless x=0 & Y=1, meaning Q has the largest impact on the functionality of the circuit



Given: T-FF w/ EN & combinational logic

Find: Design a DFF. Show work and include schematic


Solution:

D	$Q_n$	$Q^*$	T
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

T	$Q_n$
0	0
1	1


$$T = \bar{D}Q_n + D\bar{Q}_n$$

$$T = D \oplus Q_n$$

 



Given: State machine

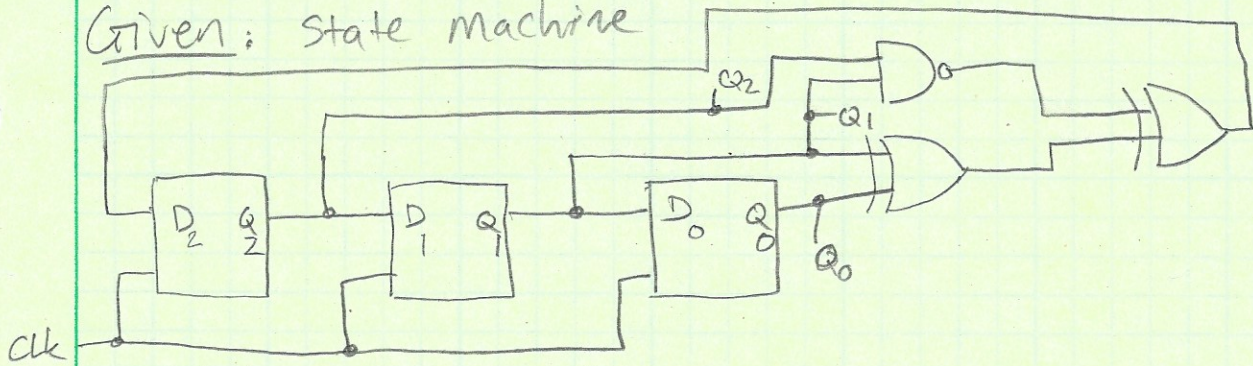

Find: excitation equations & state transition table

Solution:


$$D_0 = Q_1 \quad \& \quad D_1 = Q_2 \quad \& \quad D_2 = (Q_0 \oplus Q_1) \oplus \overline{(Q_1 Q_2)}$$

$Q_2$	$Q_1$	$Q_0$	$D_2$	$D_1$	$D_0$
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	1	1	1
1	1	1	0	1	1



Given: Determine and discuss a situation where  
Find: the output of a D-latch may become metastable. To what timing specification of a D-latch does this situation relate?

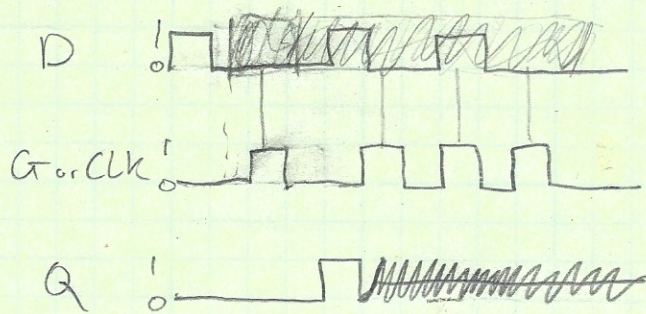Solution: If the CLK pulses too fast, it will cause a constant setup- & hold-time window, which will send Q output into metastability, until the CLK slows down.



Metastability can also happen with high frequency circuits, which is more common nowadays and why dynamic latches are more widely used.