

Given: Write AVR instructions that put the ASCII value for your initials (PN) starting at SRAM memory address 0x0100


Find: ASCII value for PN, write code to insert this ASCII value into SRAM 0x0100

Solution:

AVR Code

```
clr r26  
clr r27  
ldi r26, 80  
ldi r27, 78  
sts 0x0100, r26  
sts 0x0101, r27
```

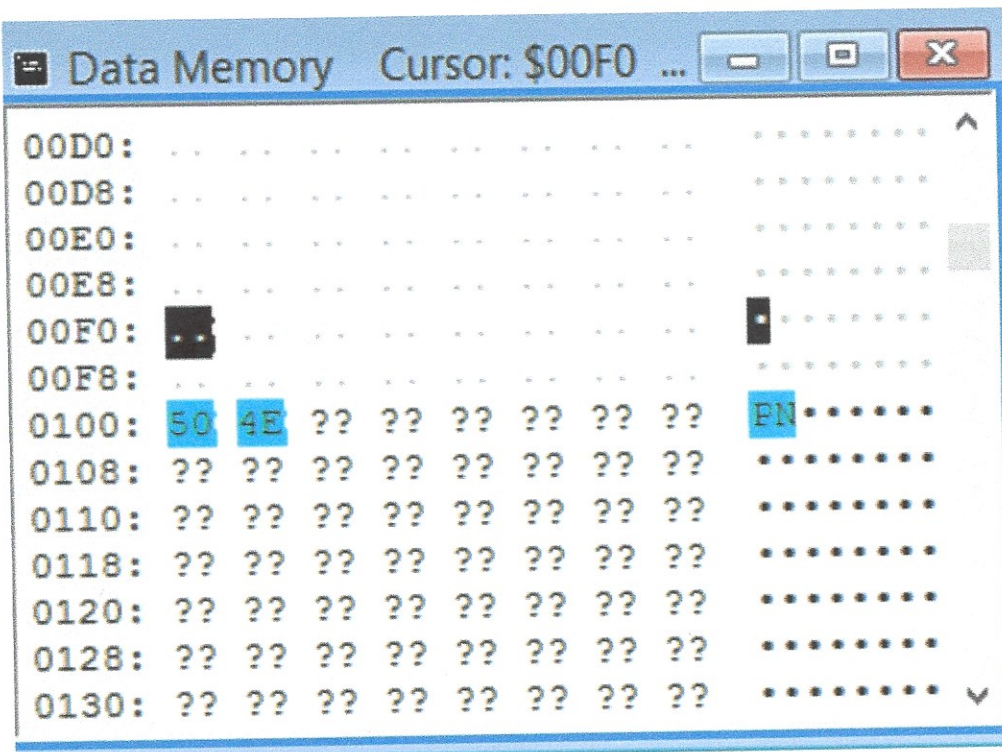
Screenshot of affected SRAM memory after code runs



Given: One 7474 D-Flip Flop

Find: Design an SR-Latch using only the given components

Solution:

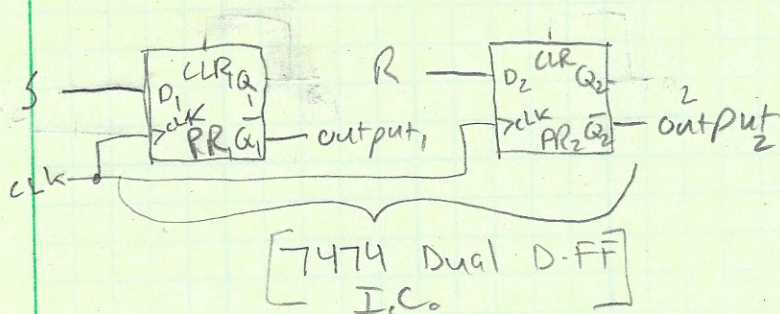

7474 I.C.T-Table 1

D	CLK	Q	\bar{Q}	when CLR is 1, Q \bar{Q} is 0 0
0	↑	0	1	
1	↑	1	0	
X	0	[last Q]	[last \bar{Q}]	
X	1	[last Q]	[last \bar{Q}]	

T-Table 3, Above Setup

clk	S	R	CLR ₁	CLR ₂	Q ₁	\bar{Q}_1	Q ₂	\bar{Q}_2
0	0	0	0	0	0	1	0	1
↑	0	1	0	0	0	1	1	0
	1	0	0	0	1	0	0	1
	1	1	0	0	1	0	1	0
0	X	X						
1	X	X						

[Last Q \bar{Q}]

SR-Latch T-Table 2



S	R	Q	\bar{Q}
0	0	Last Q	Last \bar{Q}
0	1	0	1
1	0	1	0
1	1	0	0

Reading outputs @ \bar{Q} , we have

S	R	\bar{Q}_1	\bar{Q}_2
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0	0

→ last a state.

Given:

  

Find: Compare functionality of the two sequential circuits shown. Which one performs better and why?

Solution: #1 is an SR FF, which we have seen in the book and in lecture.

#2


D_1	$EN_1 = EN_2$	$O_2 = O_3$		
0	0	0	1	X
0	1	1	1	0
1	0	0	1	X
1	1	1	0	1

we only have 2 valid states on #2, which also makes it SR FF
 
#1 will perform better because #2 will have a longer propagation delay @ circled point A which can cause major issues if not adjusted for. Assuming all I.C.s are normal, out of the box, we can assume this prop delay will cause issues.

Given:

(J) V
 (K) W
 (set) X
 (reset) Y
 (clk) Z



Find: Analyze FF circuit shown. Determine and briefly describe the function of each input.

Solution:

The circuit shown is a JK Flip Flop with Set, reset, and clock

<u>Input</u>	<u>Function</u>
V	J
W	K
X	set
Y	reset
Z	clock (smtld Trigger)
"c"	Passgate


V & W are inputs for the passgates that act as J & K inputs from a JK FF

X is a set for the passgate


Y is a reset for the passgate

Z acts as an active low clock since a smtld trigger does an inversion, and feeds into the passgates as clk

This was determined from how passgates and smtld triggers operate.

 
Problem 10.8Given:

Find: Outputs of a SR-Latch [made with NOR Gates] for the given input waveforms shown in Figure X 10.8.
Assume: inputs & outputs rise & fall times are zero.
 propagation delay of a NOR = 10 ns
 time division = 10 ns

 Solution:

Problem 10.9

Given:

 


Find: Outputs of a SR-Latch [made with NOR gates] for the given input waveforms shown in Figure x10.9

Assume: \pm /0 rise & fall times = 0

Propagation delay of NOR = 10ns

Time division = 10ns

Solution:

 

This is the point that seems impossible!

@ $S=1, R=1$, the truth table says $Q \neq Q_n = 0$ but with prop delay, this "skips"?