


Philip Nevins
5/9/2022
ENGR 271

HW#4, Problem #1

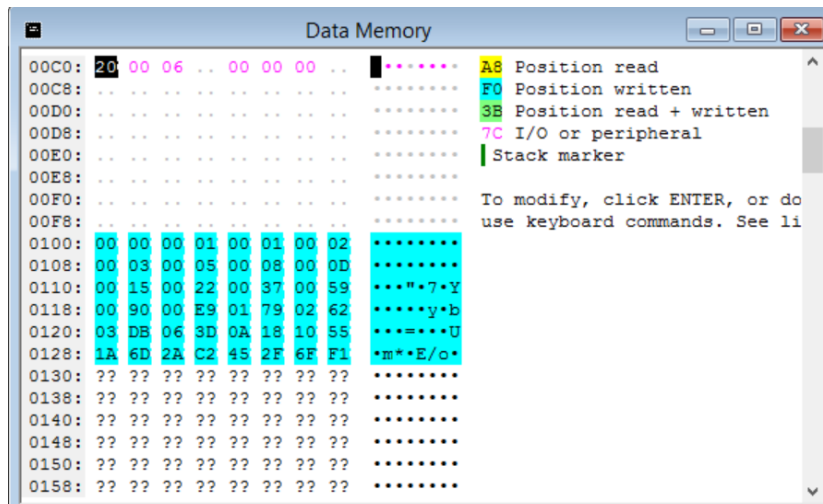1. There is a sequence of numbers called the Fibonacci sequence: 0, 1, 1, 2, 3, 5, 8, 13, 21, 34, 55, 89, 144,... (see: <https://oeis.org/A000045>). Using VMLAB write a short AVR program to calculate and move the numbers into SRAM memory starting at address 0x100. Use two bytes per number. The fourth number is 2, so the memory address 0x106 should have the byte 0x00 and address 0x107 should have the byte 0x02 (big-endian). Stop when the numbers no longer fit in two bytes.

```
.include "C:\VMLAB\include\m168def.inc"

ldi r26, 0
ldi r27, 1
ldi r16, 0
ldi r17, 0
ldi r18, 0
ldi r19, 1                ;initialize values
loop1:                    ;loop to do fib calculations
    st x+, r16
    st x+, r17
    add r17, r19
    adc r16, r18
    st x+, r18
    st x+, r19
    add r19, r17
    adc r18, r16
    brcc loop1
```




Given: Use a 74163 IC & any other combinational logic required to design a counter circuit that counts the following 11 states. 4, 5, 6, ..., 13, 14, 4

Find: Design counter [modulo-11]

Solution:

Modulo-11

| | |
|-----|------|
| (4) | 0100 |
| 5 | 0101 |
| 6 | 0110 |
| 7 | 0111 |
| 8 | 1000 |
| 9 | 1001 |
| 10 | 1010 |
| 11 | 1011 |
| 12 | 1100 |
| 13 | 1101 |
| 14 | 1110 |

 

(when out = 1110, triggers 0 \rightarrow \overline{LD} , triggers 1 \rightarrow \overline{CLR})

in C — VCC

From datasheet, when $\overline{LD} = 0$ & $\overline{CLR} = 1$, it's the preset data mode, & it loads ABCD. Since 4 (0100) is lowest #, C \rightarrow VCC.

This also matches with doing the math to calculate modulo-11 \Rightarrow (output) - (VCC input ties)
 $15 - 4 = 11 \checkmark$

We can also put 2 inverters (Z) to ensure \overline{CLR} triggers first, then the 1s value is loaded.

Given: create an unambiguous state diagram for "sticky counter" state machine, with S_0 - S_7 . Besides CLK, inputs \rightarrow RST, EN and output - DONE. Machine goes to S_0 when RST is High. RST $\&$ AND EN \rightarrow next state. Once it gets to S_7 , stays unless RST = 1. DONE = 1 if only in state S_7 & EN = 1.

Find: State Diagram


Solution:

RST \cdot EN = next state
 $S_7 \cdot$ RST = S_0
 $S_7 \cdot$ EN = DONE

INPUT: RST, EN
 CLK

Output: DONE

values: CLK/RST/EN/
 DONE

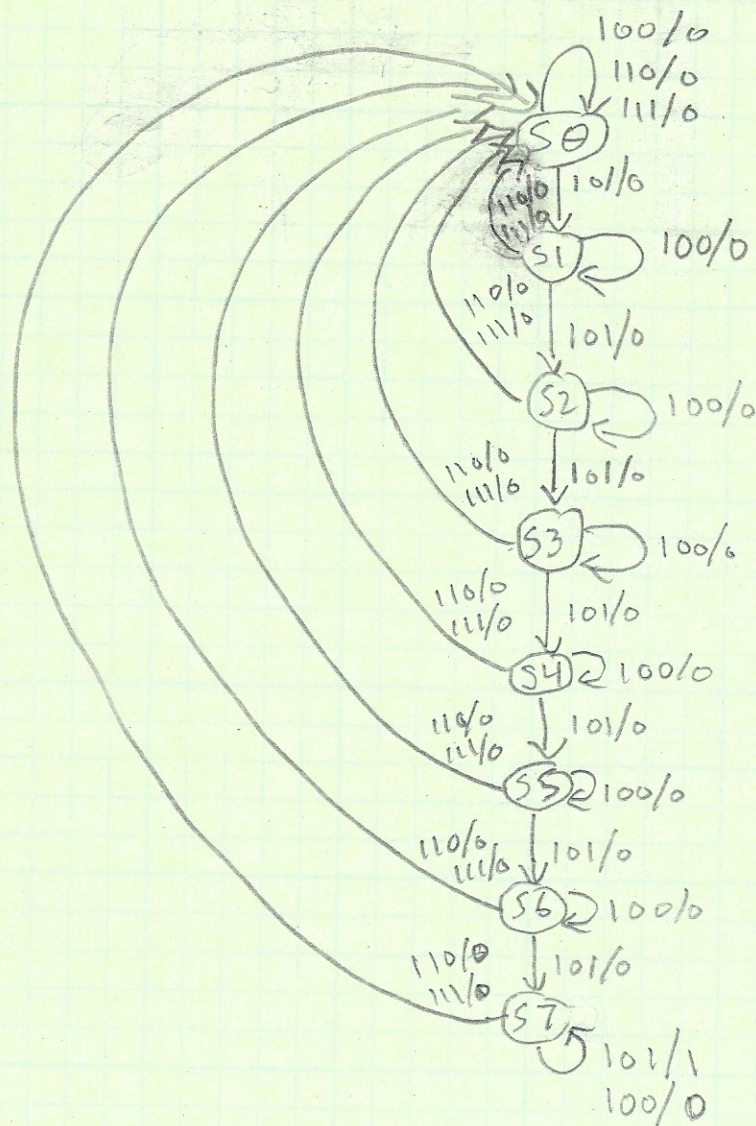


Given: Consider adjacency diagram w/ odd # states in a ring. If min. # state bits is used, is it possible to assign state bits w/o critical racing signals?

Find:

Solution: Let's consider 3 states, 2 qbits.

We set $S_0 = 00$, $S_1 = 01$ so we have no racing errors. If we set $S_2 = 11$ to have no racing error at $S_1 \rightarrow S_2$, we have one at $S_2(11) \rightarrow S_0(00)$. If we set $S_2 = 10$, we have a racing error at $S_1(01) \rightarrow S_2(10)$.

Let's consider 5 states, 3 qbits.

 

We set S_0, S_2-4 as follows in fig 1. Our only options open are 001, 011, 101, 111. To eliminate racing error $S_0 \rightarrow S_1$, $S_1 = 001$ only. All other options put a racing error $S_0 \rightarrow S_1$.

Now (001) won't work to eliminate racing errors at $S_1(001) \rightarrow S_2(010)$. This instance of having 1 racing error always occurs when we have an odd # of states.

Given: Design a counter w/ Jk FF to produce the following binary sequence: 9, 12, 11, 13, 15, 14, 10, 9...

Find: Design counter (show all design procedure steps)

Solution: Largest # = 15 \Rightarrow 1111 \therefore we need 4 FFs

| | Present | | | | Next | | | | J_4 K_4 | | J_3 K_3 | | J_2 K_2 | | J_1 K_1 | |
|----|---------|-------|-------|-------|---------|---------|---------|---------|-------------|---|-------------|---|-------------|---|-------------|---|
| | Q_4 | Q_3 | Q_2 | Q_1 | Q_4^* | Q_3^* | Q_2^* | Q_1^* | | | | | | | | |
| 9 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | X | 0 | 1 | X | 0 | X | X | 1 |
| 12 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | X | 0 | X | 1 | 1 | X | 1 | X |
| 11 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | X | 0 | 1 | X | X | 1 | X | 0 |
| 13 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | X | 0 | X | 0 | 1 | X | X | 0 |
| 15 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | X | 0 | X | 0 | X | 0 | X | 1 |
| 14 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | X | 0 | X | 1 | X | 0 | 0 | X |
| 10 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | X | 0 | 0 | X | X | 1 | 1 | X |

$P \Rightarrow N$

$1 \rightarrow 1$ JX, K0

$0 \rightarrow 1$ J1, KX

$P \Rightarrow N$

$0 \rightarrow 0$ J0, KX

$1 \rightarrow 0$ JX, K1

Using Jk FF truth table

$$J_4 = X, K_4 = 0$$

J_3

| $Q_4 Q_3$ | $Q_2 Q_1$ | 00 | 01 | 11 | 10 |
|-----------|-----------|----|-----------------|-----------------|-----------------|
| 00 | | 0 | 1 | 3 | 2 |
| 01 | | 4 | 5 | 7 | 6 |
| 11 | | X | X ¹³ | X ¹⁵ | X ¹⁴ |
| 10 | | X | 1 ⁹ | 1 ¹¹ | 10 |

$$J_3 = Q_4 Q_1$$

K_3

| $Q_4 Q_3$ | $Q_2 Q_1$ | 00 | 01 | 11 | 10 |
|-----------|-----------|----|----|----|----|
| 00 | | | | | |
| 01 | | | | | |
| 11 | | 1 | | | 1 |
| 10 | | | X | X | X |

$$K_3 = Q_4 Q_3 \bar{Q}_1$$

J_2

| $Q_4 Q_3$ | $Q_2 Q_1$ | 00 | 01 | 11 | 10 |
|-----------|-----------|----|----|----|----|
| 00 | | | | | |
| 01 | | | | | |
| 11 | | 1 | 1 | X | X |
| 10 | | | X | | X |

$$J_2 = Q_4 Q_3$$

K_2

| $Q_4 Q_3$ | $Q_2 Q_1$ | 00 | 01 | 11 | 10 |
|-----------|-----------|----|----|----|----|
| 00 | | | | | |
| 01 | | | | | |
| 11 | | X | X | | |
| 10 | | | X | 1 | 1 |

$$K_2 = Q_4 \bar{Q}_3 Q_2$$

| J_1 $Q_4 Q_3$ | $Q_2 Q_1$ | | | |
|--------------------|-----------|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | | | | |
| 01 | | | | |
| 11 | 1 | x | x | |
| 10 | | x | x | 1 |

$$J_1 = Q_4 Q_3 \bar{Q}_2 \bar{Q}_1 + Q_4 \bar{Q}_3 Q_2 \bar{Q}_1$$

$$J_1 = Q_4 \bar{Q}_1 (Q_3 \oplus Q_2)$$

| K_1 $Q_4 Q_3$ | $Q_2 Q_1$ | | | |
|--------------------|-----------|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | | | | |
| 01 | | | | |
| 11 | x | | 1 | x |
| 10 | | 1 | | x |

$$K_1 = Q_4 \bar{Q}_3 \bar{Q}_2 Q_1 + Q_4 Q_3 Q_2 Q_1$$

$$K_1 = Q_4 Q_1 (Q_3 \oplus Q_2)$$

